

**ANSWERS**

**Level 1:** To solve this question, we need to use the equation to find capacitive reactance.

$$X_c = -\frac{1}{2\pi fC}$$

We were given both values; we know that  $f$  is equal to 60 Hz, and  $C$  is equal to  $2 \times 10^{-6}$  farads. Let's plug those values into that equation.

$$X_c = -\frac{1}{2 * \pi * 60 * (2 * 10^{-6})}$$

$$X_c = -\frac{1}{0.000754}$$

$$X_c = -1,326 \Omega$$

Wow! We get a huge reactance from a small capacitor. Remember, this reactance is negative. Usually, we want zero reactance in our system, so any amount of reactance, positive or negative, will mean that we are wasting power.

**Level 2:** Solving this question requires setting up an equation where the combination of inductive reactance and capacitive reactance balances out to give zero total reactance.

$$0 = X_L + X_c$$

Now, let's replace those reactance values with the equations from earlier.

$$0 = 2\pi fL + -\frac{1}{2\pi fC}$$

Now we can do some slight shifting of the variables to make everything simpler.

$$\frac{1}{2\pi fC} = 2\pi fL$$

At this point, we've completed a small proof! We now know that whenever we want a zero reactance system, the capacitive reactance must be exactly equal to the inductive reactance.

We can now substitute in the values given to us to find the inductance we want.

$$\frac{1}{2 * \pi * 50 * (12 * 10^{-3})} = 2 * \pi * 50 * L$$

$$0.265 = 314.16 * L$$

$$0.000844 \text{ H} = L$$

A small inductance makes a lot of sense. We put in a small capacitor, so we need a small inductor to balance out that capacitive reactance.



Knowing what creates reactance is important, because reactance plays a big part in power factor. A power factor with less reactance, and therefore less reactive power, means a more efficient load!